

## CAD 最終課題

-64 点高速フーリエ変換回路-

### レポート提出者

055702B 池野谷克俊

(チーム名: complete)

所属: 琉球大学工学部情報工学科学部 2 年

T シャツ希望サイズ: M

### チームメンバー

池野谷克俊 (学籍番号: 055702B) j05002@ie.u-ryukyu.ac.jp

金城佑典 (学籍番号: 055717A) j05017@ie.u-ryukyu.ac.jp

2007 年 2 月 21 日 (水)

## 目次

<b>1</b>	<b>構成と動作</b>	<b>2</b>
1.1	FFT64 . . . . .	2
1.2	TWIDDLE . . . . .	2
1.3	複素乗算器 (Cmult と multar) . . . . .	3
1.4	Stage1 . . . . .	4
1.5	Stage2 . . . . .	4
1.6	Stage3 . . . . .	5
1.7	REORDER . . . . .	6
<b>2</b>	<b>完成した回路</b>	<b>6</b>
2.1	性能 . . . . .	6
2.2	動作確認 . . . . .	7
2.2.1	1) ALL1 入力 . . . . .	7
2.2.2	2) 1 周期する複素回転信号 初期値=1+0j . . . . .	7
2.2.3	3) 1 周期する複素回転信号 初期値=0-1j . . . . .	8
2.2.4	4) 1 周期する COS 信号 . . . . .	8
2.2.5	5) 15 周期する複素回転信号 . . . . .	8
<b>3</b>	<b>工夫した点</b>	<b>9</b>
<b>4</b>	<b>自由意見</b>	<b>9</b>
<b>5</b>	<b>VHDL のコード (全文)</b>	<b>10</b>
5.1	fft64.vhd . . . . .	10
5.2	twiddle.vhd . . . . .	11
5.3	cmult.vhd . . . . .	12
5.4	multar.vhd . . . . .	13
5.5	stage1.vhd . . . . .	13
5.6	stage2.vhd . . . . .	16
5.7	stage3.vhd . . . . .	18
5.8	reorder.vhd . . . . .	20

# 1 構成と動作

## 1.1 FFT64

$$X(k) = \sum_{n=0}^{63} x(n)e^{-j\left(\frac{2\pi}{64}\right)nk} = \sum_{n=0}^{63} x(n)W_{64}^{nk} \quad (k = 0, 1, 2, \dots, 63)$$

の演算を行う

FFT64は64点高速フーリエ変換を行う回路で、複素数の演算を行う「Stage1」「Stage2」「Stage3」と演算中に入れ代わってしまった順番をもとに戻す「REORDER」から構成されている。

 


図 1: FFT64 のブロック図

「Stage1」「Stage2」「Stage3」は図のようにそれぞれ4つの複素数から4つの演算結果を出すことができるが、上から順番に計算していきたいので shift 動作を繰り返すことで 0 ~ 63 まで合計 64 点の演算を行い、「REORDER」によって順序を入れ替えた結果を出力として返す。

## 1.2 TWIDDLE

Twiddle の生成を行う回路、Stage1, Stage2, Stage3 で使用する

$$W_{64} = e^{-j\frac{2\pi}{64}}$$

の演算を行うが、ここで

$$e^{j\theta} = \cos\theta + j\sin\theta$$

より

$$W_{64} = e^{-j\frac{2\pi}{64}} = \cos\frac{2\pi}{64} + j\sin\frac{2\pi}{64}$$

なので、実際にはあらかじめ計算しておいた  $\cos$  の数値のリストから要求されたものを出力するだけの回路になっている ( $\sin$  の数値は  $\cos$  の数値から得られる)

### 1.3 複素乗算器 (Cmult と multar)

複素数の乗算を行う回路、Stage1,Stage2,Stage3 で使用する

$$(AIN\_I + jAIN\_Q) * (BIN\_I + jBIN\_Q)$$

$$= \{(AIN\_I * BIN\_I) - (AIN\_Q * BIN\_Q)\} + j\{(AIN\_Q * BIN\_I) + (AIN\_I * BIN\_Q)\}$$

の計算を行う

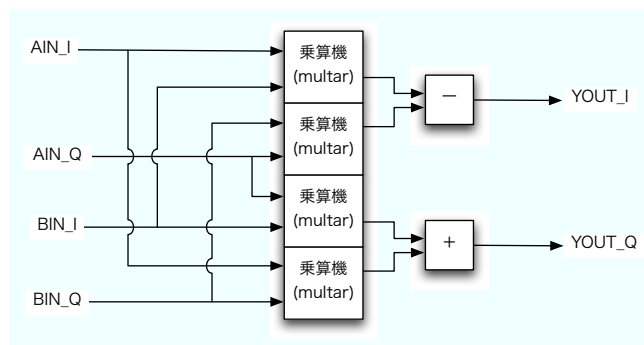


図 2: Cmult のブロック図

図中の乗算機は multar(multar.vhd) で実装されている。

### 1.4 Stage1

x 信号を用いて

$$x1(n_0 + 4n_1 + 16k_0) = \begin{pmatrix} x(n_0 + 4n_1) \\ +(-j)^{k_1}x(n_0 + 4n_1 + 16) \\ +(-1)^{k_1}x(n_0 + 4n_1 + 32) \\ +(j)^{k_1}x(n_0 + 4n_1 + 48) \end{pmatrix} W_{64}^{k_0(n_0+4n_1)}$$

の演算を受け持つ回路

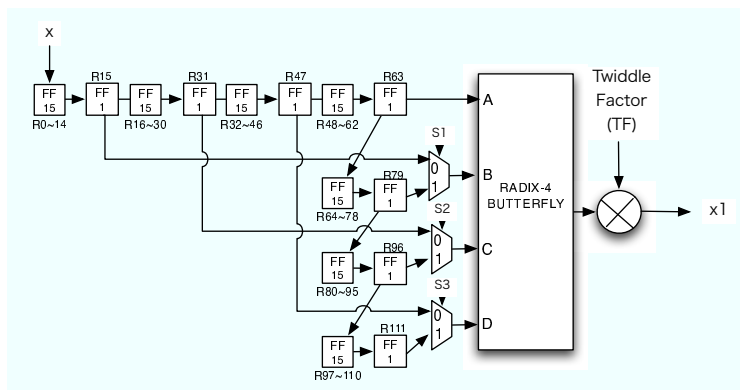


図 3: Stage1 のブロック図

### 1.5 Stage2

x1 信号を用いて

$$x2(n_0 + 4k_1 + 16k_0) = \begin{pmatrix} x1(n_0 + 0 + 16k_0) \\ +(-j)^{k_1}x1(n_0 + 4 + 16k_0) \\ +(-1)^{k_1}x1(n_0 + 8 + 16k_0) \\ +(j)^{k_1}x1(n_0 + 12 + 16k_0) \end{pmatrix} W_{16}^{(k_1 n_0)}$$

の演算を行う回路

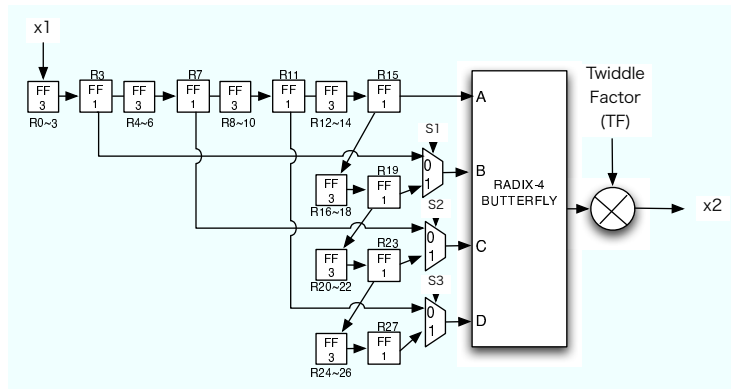


図 4: Stage2 のブロック図

## 1.6 Stage3

$x_2$  信号を用いて

$$\begin{aligned}
 x_3(k_2 + 4k_1 + 16k_0) &= \sum_{n_0=0}^3 x_2(n_0 + 4k_1 + 16k_0) W_4^{n_0 k_2} \\
 &= \begin{pmatrix} x_2(0 + 4k_1 + 16k_0) \\ +x_2(1 + 4k_1 + 16k_0) W_4^{k_2} \\ +x_2(2 + 4k_1 + 16k_0) W_4^{2k_2} \\ +x_2(3 + 4k_1 + 16k_0) W_4^{3k_2} \end{pmatrix} \\
 &= \begin{pmatrix} x_2(0 + 4k_1 + 16k_0) \\ +(-j)^{k_2} x_2(1 + 4k_1 + 16k_0) \\ +(-1)^{k_1} x_2(2 + 4k_1 + 16k_0) \\ +(j)^{k_2} x_2(3 + 4k_1 + 16k_0) \end{pmatrix}
 \end{aligned}$$

の演算を行う回路

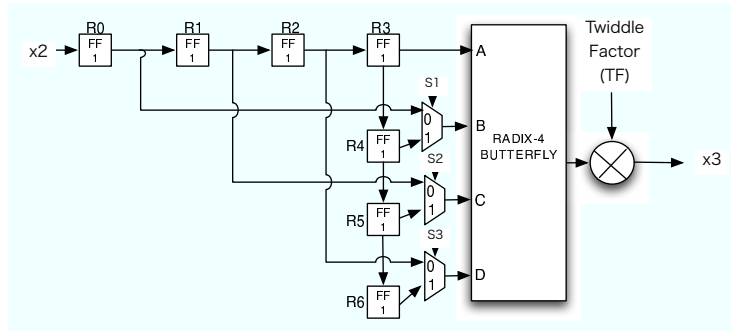


図 5: Stage3 のブロック図

## 1.7 REORDER

x3 信号を並べ替えて X 信号を出力する回路

Stage1, Stage2, Stage3 によって x 信号から x3 信号への変換はできたが、計算された数字列の順序が異なっている。

$$X(k_0 + 4k_1 + 16k_2) = x3(k_2 + 4k_1 + 16k_0)$$

そこで右の図のようにして x3 信号（左図黄色）を正しい答えである X 信号（左図赤色）のように演算結果を並べ替える

0	0	16	1	32	2	48	3
1	16	17	17	33	18	49	19
2	32	18	33	34	34	50	35
3	48	19	49	35	50	51	51
4	4	20	5	36	6	52	7
5	20	21	21	37	22	53	23
6	36	22	37	38	38	54	39
7	52	23	53	39	54	55	55
8	8	24	9	40	10	56	11
9	24	25	25	41	26	57	27
10	40	26	41	42	42	58	43
11	56	27	57	43	58	59	59
12	12	28	13	44	14	60	15
13	28	29	29	45	30	61	31
14	44	30	45	46	46	62	47
15	60	31	61	47	62	63	63

図 6: Reorder

 


図 7: Reorder による順番の入れ替え

## 2 完成した回路

### 2.1 性能

クリティカルパスのスピード

$dataarrivaltime : 49.20$  なので  $49.20/1.195 = 41.1715481$  よりクリティカルパスのスピードは  $41.17UNIT\_DELAY$

## 論理合成後の回路規模

$Totalcellarea : 95521.000000$  なので  $95521/3 = 31840.3333$  より回路面積は  $31840.34UNIT\_AREA$

## 2.2 動作確認

### 2.2.1 1) ALL1 入力

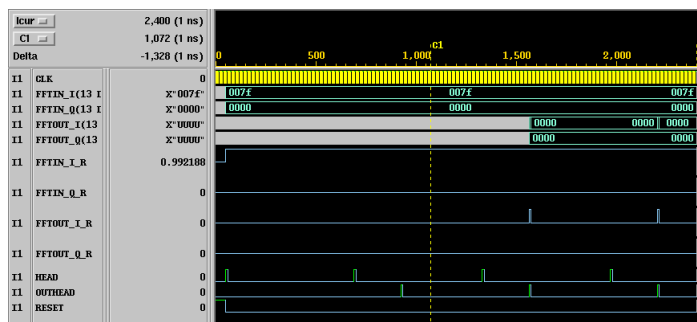


図 8: ALL1 入力の動作波形

### 2.2.2 2) 1 周期する複素回転信号 初期値=1+0j

 


図 9: 1 周期する複素回転信号 初期値=1+0j の動作波形



### 2.2.3 3) 1周期する複素回転信号 初期値=0-1j

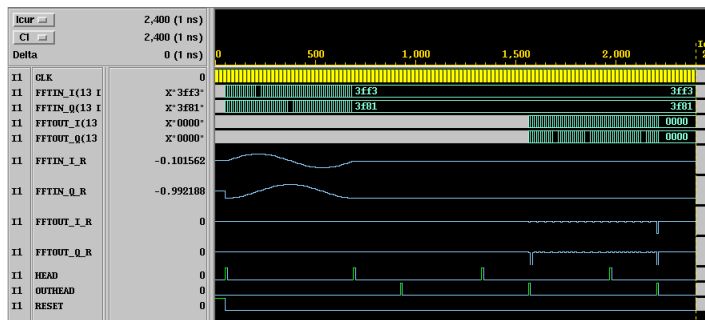


図 10: 1周期する複素回転信号 初期値=0-1j の動作波形

### 2.2.4 4) 1周期する COS 信号

 


図 11: 1周期する COS 信号の動作波形

### 2.2.5 5) 15周期する複素回転信号

 


図 12: 15周期する複素回転信号の動作波形

### 3 工夫した点

stage1.vhd と stage2.vhd において、PHASE GENERATOR と TWIDDLE FACTOR GENERATOR を if 文や case 文などを用いずに、64 CYCLE COUNTER の信号 (COUNT) 等を用いて、できるだけ短い記述で表せるように工夫した。以下にその部分を示す。

- stage1.vhd の抜粋

```
-- PHASE GENERATOR
    PHASE <= COUNT(5 downto 4); --henkou

-- TWIDDLE FACTOR GENERATOR
    TF <= unsigned(COUNT(3 downto 0)) * unsigned(PHASE(1 downto 0)); --henkou
```

- stage2.vhd の抜粋

```
-- PHASE GENERATOR
    PHASE <= COUNT(3 downto 2); --henkou

-- TWIDDLE FACTOR GENERATOR
    TF <= unsigned(COUNT(1 downto 0)) * (unsigned(PHASE(1 downto 0)) & "00"); --henkou
```

### 4 自由意見

最終課題の内容はかなり難しかったが、ほぼ完成されたソースをくれたので、なんとか完成させることができた。なので、総合的に見たら良いレベルの課題だったと思う。また、stage1.vhd と stage2.vhd の PHASE GENERATOR と TWIDDLE FACTOR GENERATOR の部分は、短い記述で実現できたので、けっこう満足している。

## 5 VHDLのコード(全文)

### 5.1 fft64.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity FFT64 is
  port (
    RESET      : in  std_logic;
    CLK        : in  std_logic;
    HEAD       : in  std_logic;
    FFTIN_I    : in  std_logic_vector(13 downto 0); -- <14,6,t>
    FFTIN_Q    : in  std_logic_vector(13 downto 0); -- <14,6,t>
    OUTHEAD    : out std_logic;
    FFTOUT_I   : out std_logic_vector(13 downto 0); -- <14,6,t>
    FFTOUT_Q   : out std_logic_vector(13 downto 0); -- <14,6,t>
  );
end;

architecture RTL of FFT64 is

  component STAGE1 is
    port (
      RESET      : in  std_logic;
      CLK        : in  std_logic;
      S1HEAD     : in  std_logic;
      S1IN_I     : in  std_logic_vector(13 downto 0); -- <14,6,t>
      S1IN_Q     : in  std_logic_vector(13 downto 0); -- <14,6,t>
      S1OUTHEAD  : out std_logic;
      S1OUT_I    : out std_logic_vector(13 downto 0); -- <14,6,t>
      S1OUT_Q    : out std_logic_vector(13 downto 0); -- <14,6,t>
    );
  end component;

  component STAGE2 is
    port (
      RESET      : in  std_logic;
      CLK        : in  std_logic;
      S2HEAD     : in  std_logic;
      S2IN_I     : in  std_logic_vector(13 downto 0); -- <14,6,t>
      S2IN_Q     : in  std_logic_vector(13 downto 0); -- <14,6,t>
      S2OUTHEAD  : out std_logic;
      S2OUT_I    : out std_logic_vector(13 downto 0); -- <14,6,t>
      S2OUT_Q    : out std_logic_vector(13 downto 0); -- <14,6,t>
    );
  end component;

  component STAGE3 is
    port (
      RESET      : in  std_logic;
      CLK        : in  std_logic;
      S3HEAD     : in  std_logic;
      S3IN_I     : in  std_logic_vector(13 downto 0); -- <14,6,t>
      S3IN_Q     : in  std_logic_vector(13 downto 0); -- <14,6,t>
      S3OUTHEAD  : out std_logic;
      S3OUT_I    : out std_logic_vector(13 downto 0); -- <14,6,t>
      S3OUT_Q    : out std_logic_vector(13 downto 0); -- <14,6,t>
    );
  end component;

  component REORDER
    port (
      RESET      : in  std_logic;
    );
  end component;
```

```

        CLK      : in  std_logic;
        ROHEAD   : in  std_logic; -- <1,1,u>
        ROIN_I   : in  std_logic_vector(13 downto 0); -- <14,6,t>
        ROIN_Q   : in  std_logic_vector(13 downto 0); -- <14,6,t>
        ROOUTHEAD : out std_logic; -- <1,1,u>
        ROOUT_I  : out std_logic_vector(13 downto 0); -- <14,6,t>
        ROOUT_Q  : out std_logic_vector(13 downto 0)); -- <14,6,t>
end component;

signal S1HEAD, S1OUTHEAD : std_logic;
signal S2HEAD, S2OUTHEAD : std_logic;
signal S3HEAD, S3OUTHEAD : std_logic;
signal ROHEAD, ROOUTHEAD : std_logic;
signal S1IN_I, S1IN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal S1OUT_I, S1OUT_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal S2IN_I, S2IN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal S2OUT_I, S2OUT_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal S3IN_I, S3IN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal S3OUT_I, S3OUT_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal ROIN_I, ROIN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal ROOUT_I, ROOUT_Q : std_logic_vector (13 downto 0); -- <14,6,t>

begin

S1HEAD <= HEAD; S1IN_I <= FFTIN_I; S1IN_Q <= FFTIN_Q;

ST1: STAGE1 port map (RESET, CLK, S1HEAD, S1IN_I, S1IN_Q, S1OUTHEAD, S1OUT_I, S1OUT_Q);

S2HEAD <= S1OUTHEAD; S2IN_I <= S1OUT_I; S2IN_Q <= S1OUT_Q;

ST2: STAGE2 port map (RESET, CLK, S2HEAD, S2IN_I, S2IN_Q, S2OUTHEAD, S2OUT_I, S2OUT_Q);

S3HEAD <= S2OUTHEAD; S3IN_I <= S2OUT_I; S3IN_Q <= S2OUT_Q;

ST3: STAGE3 port map (RESET, CLK, S3HEAD, S3IN_I, S3IN_Q, S3OUTHEAD, S3OUT_I, S3OUT_Q);

ROHEAD <= S3OUTHEAD; ROIN_I <= S3OUT_I; ROIN_Q <= S3OUT_Q;

R00: REORDER port map (RESET, CLK, ROHEAD, ROIN_I, ROIN_Q, ROOUTHEAD, ROOUT_I, ROOUT_Q);

OUTHEAD <= ROOUTHEAD; FFTOUT_I <= ROOUT_I; FFTOUT_Q <= ROOUT_Q;

end;

```

## 5.2 twiddle.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity TWIDDLE is
    port (
        ADDR : in  std_logic_vector(5 downto 0); -- <6,6,u>
        W_I  : out std_logic_vector(9 downto 0); -- <10,0,t>
        W_Q  : out std_logic_vector(9 downto 0)); -- <10,0,t>
end;

architecture RTL of TWIDDLE is
begin
    process (ADDR)

```

```

variable iaddr : integer;
variable qaddr : integer;
type rom_type is array(0 to 63) of std_logic_vector(9 downto 0);
constant cos_table : rom_type := (
"0111111111","0111111110","0111110110","0111101010",
"0111011001","0111000100","0110101010","0110001100",
"0101101010","0101000101","0100011100","0011110001",
"0011000100","0010010101","0001100100","0000110010",
"0000000000","1111001110","1110011100","1101101011",
"1100111100","1100001111","1011100100","1010111011",
"1010010110","1001110100","1001010110","1000111100",
"1000100111","1000010110","1000001010","1000000010",
"1000000000","1000000010","1000001010","1000010110",
"1000100111","1000111100","1001010110","1001110100",
"1010010110","1010111011","1011100100","1100001111",
"1100111100","1101101011","1110011100","1111001110",
"0000000000","0000110010","0001100100","0010010101",
"0011000100","0011110001","0100011100","0101000101",
"0101101010","0110001100","0110101010","0111000100",
"0111011001","0111101010","0111110110","0111111110"
);

begin
iaddr := conv_integer(unsigned(ADDR));
qaddr := conv_integer(unsigned(ADDR)+16);
W_I <= cos_table(iaddr);
W_Q <= cos_table(qaddr);
end process;

end;

```

### 5.3 cmult.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

entity CMULT is
port(AIN_I      : in  std_logic_vector(13 downto 0); -- <14,6,t>
      AIN_Q      : in  std_logic_vector(13 downto 0); -- <14,6,t>
      BIN_I      : in  std_logic_vector(9  downto 0); -- <10,0,t>
      BIN_Q      : in  std_logic_vector(9  downto 0); -- <10,0,t>
      YOUT_I     : out std_logic_vector(13 downto 0); -- <14,6,t>
      YOUT_Q     : out std_logic_vector(13 downto 0)); -- <14,6,t>
end CMULT;

architecture RTL of CMULT is

-- component declaration
component MULTAR
port(in1      : in  std_logic_vector(13 downto 0); -- <14,6,t>
      in2      : in  std_logic_vector(9  downto 0); -- <10,0,t>
      outp     : out std_logic_vector(13 downto 0)); -- <14,6,t>
end component;

signal S1, S2, S3, S4 : std_logic_vector(13 downto 0); -- <14,6,t>

begin

M1: MULTAR port map (AIN_I, BIN_I, S1);

```

```

M2: MULTAR port map (AIN_Q, BIN_Q, S2);
M3: MULTAR port map (AIN_Q, BIN_I, S3);
M4: MULTAR port map (AIN_I, BIN_Q, S4);

YOUT_I <= signed(S1) - signed(S2);
YOUT_Q <= signed(S3) + signed(S4);

end RTL;

```

## 5.4 multar.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

entity MULTAR is
  port(in1      : in  std_logic_vector(13 downto 0); -- <14,6,t>
        in2      : in  std_logic_vector(9  downto 0); -- <10,0,t>
        outp     : out std_logic_vector(13 downto 0)); -- <14,6,t>
end MULTAR;

architecture RTL of MULTAR is

begin

  MULTAR : process(in1,in2)
    variable var_tprod : std_logic_vector(23 downto 0); -- <24,7,t>
    variable var_round : std_logic_vector(13 downto 0); -- <14,6,t>
  begin
    var_tprod := signed(in1) * signed(in2);

    if (var_tprod(8) = '1') then
      var_round := signed(var_tprod(22 downto 9)) + '1';
    else
      var_round := var_tprod(22 downto 9);
    end if;

    outp <= var_round;

  end process MULTAR;

end RTL;

```

## 5.5 stage1.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity STAGE1 is
  port (
    RESET      : in  std_logic;
    CLK        : in  std_logic;
    S1HEAD     : in  std_logic; -- <1,1,u>
    S1IN_I     : in  std_logic_vector(13 downto 0); -- <14,6,t>
    S1IN_Q     : in  std_logic_vector(13 downto 0); -- <14,6,t>
    S1OUTHEAD  : out std_logic; -- <1,1,u>
    S1OUT_I    : out std_logic_vector(13 downto 0); -- <14,6,t>
  );
end STAGE1;

```

```

        S1OUT_Q : out std_logic_vector(13 downto 0)); -- <14,6,t>
end;

architecture RTL of STAGE1 is

component CMULT is
    port(AIN_I : in std_logic_vector(13 downto 0); -- <14,6,t>
          AIN_Q : in std_logic_vector(13 downto 0); -- <14,6,t>
          BIN_I : in std_logic_vector(9  downto 0); -- <10,0,t>
          BIN_Q : in std_logic_vector(9  downto 0); -- <10,0,t>
          YOUT_I : out std_logic_vector(13 downto 0); -- <14,6,t>
          YOUT_Q : out std_logic_vector(13 downto 0)); -- <14,6,t>
end component;

component TWIDDLE
    port (
        ADDR : in std_logic_vector(5 downto 0); -- <6,6,u>
        W_I  : out std_logic_vector(9  downto 0); -- <10,0,t>
        W_Q  : out std_logic_vector(9  downto 0)); -- <10,0,t>
end component;

signal HEAD : std_logic_vector(64 downto 0); -- 65 FFs for Head Signal Delay
signal COUNT : std_logic_vector(5  downto 0); -- count 0 to 63 cycles
signal PHASE : std_logic_vector(1  downto 0); -- PHASE 0 to 3
signal TF : std_logic_vector(5  downto 0); -- TWIDDLE FACTOR INDEX
signal S1, S2, S3 : std_logic;

signal REGIN_I : std_logic_vector (13 downto 0); -- <14,6,t>
signal REGIN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
type shiftreg112 is array (0 to 111) of std_logic_vector (13 downto 0); -- <14,6,t>
signal REG_I : shiftreg112;
signal REG_Q : shiftreg112;
signal A_I, A_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal B_I, B_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal C_I, C_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal D_I, D_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal Y_I, Y_Q : std_logic_vector (13 downto 0); -- <14,6,t> butterfly output
signal W_I, W_Q : std_logic_vector(9  downto 0); -- <10,0,t>

begin

-- OUTHEAD GENERATION
process ( CLK, RESET ) begin
    if (RESET = '1') then
        for I in 0 to 64 loop
            HEAD(I) <= '0';
        end loop;
    elsif ( CLK'event and CLK = '1' ) then
        HEAD(0) <= S1HEAD;
        for I in 1 to 64 loop
            HEAD(I) <= HEAD(I-1);
        end loop;
    end if;
end process;
S1OUTHEAD <= HEAD(64);

-- 64 CYCLE COUNTER
process ( CLK, RESET ) begin
    if (RESET = '1') then
        COUNT <= "000000";
    elsif ( CLK'event and CLK = '1' ) then
        if (S1HEAD = '1') then

```

```

        COUNT <= "000000";
    else
        COUNT <= unsigned(COUNT) + '1';
    end if;
end if;
end process;

-- PHASE GENERATOR
PHASE <= COUNT(5 downto 4); --henkou

-- TWIDDLE FACTOR GENERATOR
TF <= unsigned(COUNT(3 downto 0)) * unsigned(PHASE(1 downto 0)); --henkou

-- SELECT SIGNAL GENERATOR
S1 <= PHASE(0) or PHASE(1);
S2 <= PHASE(1);
S3 <= PHASE(0) and PHASE(1);

-- SHIFT REGISTER
process ( CLK ) begin
    if ( CLK'event and CLK = '1' ) then
        REGIN_I <= S1IN_I;    REGIN_Q <= S1IN_Q;
        REG_I(0) <= REGIN_I;  REG_Q(0) <= REGIN_Q;
        for I in 1 to 111 loop
            REG_I(I) <= REG_I(I-1);  REG_Q(I) <= REG_Q(I-1);
        end loop;
    end if;
end process;

-- A,B,C,D GENERATION
A_I <= REG_I(63);
A_Q <= REG_Q(63);
B_I <= REG_I(15) when S1 = '0' else REG_I(79);
B_Q <= REG_Q(15) when S1 = '0' else REG_Q(79);
C_I <= REG_I(31) when S2 = '0' else REG_I(95);
C_Q <= REG_Q(31) when S2 = '0' else REG_Q(95);
D_I <= REG_I(47) when S3 = '0' else REG_I(111);
D_Q <= REG_Q(47) when S3 = '0' else REG_Q(111);

-- RADIX-4 BUTTERFLY
process (PHASE, A_I, B_I, C_I, D_I, A_Q, B_Q, C_Q, D_Q) begin
    case PHASE is
        when "00" =>
            Y_I <= signed(A_I) + signed(B_I) + signed(C_I) + signed (D_I);
            Y_Q <= signed(A_Q) + signed(B_Q) + signed(C_Q) + signed (D_Q);
        when "01" =>
            Y_I <= signed(A_Q) + signed(B_I) - signed(C_Q) - signed (D_I);
            Y_Q <= - signed(A_I) + signed(B_Q) + signed(C_I) - signed (D_Q);
        when "10" =>
            Y_I <= signed(A_I) - signed(B_I) + signed(C_I) - signed (D_I);
            Y_Q <= signed(A_Q) - signed(B_Q) + signed(C_Q) - signed (D_Q);
        when "11" =>
            Y_I <= signed(A_Q) - signed(B_I) - signed(C_Q) + signed (D_I);
            Y_Q <= - signed(A_I) - signed(B_Q) + signed(C_I) + signed (D_Q);
        when others =>
            Y_I <= (others => 'X');
            Y_Q <= (others => 'X');
    end case;
end process;

TWO: TWIDDLE port map (TF, W_I, W_Q);

```



```
CM0: CMULT port map (Y_I, Y_Q, W_I, W_Q, S1OUT_I, S1OUT_Q);
```

```
end;
```

## 5.6 stage2.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity STAGE2 is
  port (
    RESET      : in  std_logic;
    CLK        : in  std_logic;
    S2HEAD     : in  std_logic;           -- <1,1,u>
    S2IN_I    : in  std_logic_vector(13 downto 0); -- <14,6,t>
    S2IN_Q    : in  std_logic_vector(13 downto 0); -- <14,6,t>
    S2OUTHEAD : out std_logic;           -- <1,1,u>
    S2OUT_I   : out std_logic_vector(13 downto 0); -- <14,6,t>
    S2OUT_Q   : out std_logic_vector(13 downto 0); -- <14,6,t>
  );
end;

architecture RTL of STAGE2 is

  component CMULT is
    port(AIN_I      : in  std_logic_vector(13 downto 0); -- <14,6,t>
         AIN_Q      : in  std_logic_vector(13 downto 0); -- <14,6,t>
         BIN_I      : in  std_logic_vector(9  downto 0); -- <10,0,t>
         BIN_Q      : in  std_logic_vector(9  downto 0); -- <10,0,t>
         YOUT_I     : out std_logic_vector(13 downto 0); -- <14,6,t>
         YOUT_Q     : out std_logic_vector(13 downto 0); -- <14,6,t>
    );
  end component;

  component TWIDDLE is
    port (
      ADDR : in  std_logic_vector(5 downto 0); -- <6,6,u>
      W_I  : out std_logic_vector(9  downto 0); -- <10,0,t>
      W_Q  : out std_logic_vector(9  downto 0); -- <10,0,t>
    );
  end component;

  signal HEAD : std_logic_vector(16 downto 0); -- 17 FFs for Head Signal Delay
  signal COUNT : std_logic_vector(5 downto 0); -- count 0 to 63 cycles
  signal PHASE : std_logic_vector(1 downto 0); -- PHASE 0 to 3
  signal TF : std_logic_vector(5 downto 0); -- TWIDDLE FACTOR INDEX
  signal S1, S2, S3 : std_logic;

  signal REGIN_I : std_logic_vector (13 downto 0); -- <14,6,t>
  signal REGIN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  type shiftreg28 is array (0 to 27) of std_logic_vector (13 downto 0); -- <14,6,t>
  signal REG_I : shiftreg28;
  signal REG_Q : shiftreg28;
  signal A_I, A_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  signal B_I, B_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  signal C_I, C_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  signal D_I, D_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  signal Y_I, Y_Q : std_logic_vector (13 downto 0); -- <14,6,t> butterfly output
  signal W_I, W_Q : std_logic_vector(9  downto 0); -- <10,0,t>

begin
```

```

-- OUTHEAD GENERATION
process ( CLK, RESET ) begin
  if (RESET = '1') then
    for I in 0 to 16 loop
      HEAD(I) <= '0';
    end loop;
  elsif ( CLK'event and CLK = '1' ) then
    HEAD(0) <= S2HEAD;
    for I in 1 to 16 loop
      HEAD(I) <= HEAD(I-1);
    end loop;
  end if;
end process;
S2OUTHEAD <= HEAD(16);

-- 64 CYCLE COUNTER
process ( CLK, RESET ) begin
  if (RESET = '1') then
    COUNT <= "000000";
  elsif ( CLK'event and CLK = '1' ) then
    if (S2HEAD = '1') then
      COUNT <= "000000";
    else
      COUNT <= unsigned(COUNT) + '1';
    end if;
  end if;
end process;

-- PHASE GENERATOR
PHASE <= COUNT(3 downto 2); --henkou

-- TWIDDLE FACTOR GENERATOR
TF <= unsigned(COUNT(1 downto 0)) * (unsigned(PHASE(1 downto 0)) & "00"); --henkou

-- SELECT SIGNAL GENERATOR
S1 <= PHASE(0) or PHASE(1);
S2 <= PHASE(1);
S3 <= PHASE(0) and PHASE(1);

-- SHIFT REGISTER
process ( CLK ) begin
  if ( CLK'event and CLK = '1' ) then
    REGIN_I <= S2IN_I;   REGIN_Q <= S2IN_Q;
    REG_I(0) <= REGIN_I;  REG_Q(0) <= REGIN_Q;
    for I in 1 to 27 loop
      REG_I(I) <= REG_I(I-1);  REG_Q(I) <= REG_Q(I-1);
    end loop;
  end if;
end process;

-- A,B,C,D GENERATION
A_I <= REG_I(15);
A_Q <= REG_Q(15);
B_I <= REG_I(3) when S1 = '0' else REG_I(19);
B_Q <= REG_Q(3) when S1 = '0' else REG_Q(19);
C_I <= REG_I(7) when S2 = '0' else REG_I(23);
C_Q <= REG_Q(7) when S2 = '0' else REG_Q(23);
D_I <= REG_I(11) when S3 = '0' else REG_I(27);
D_Q <= REG_Q(11) when S3 = '0' else REG_Q(27);

```

```

-- RADIX-4 BUTTERFLY

process (PHASE, A_I, B_I, C_I, D_I, A_Q, B_Q, C_Q, D_Q) begin
  case PHASE is
    when "00" =>
      Y_I <= signed(A_I) + signed(B_I) + signed(C_I) + signed (D_I);
      Y_Q <= signed(A_Q) + signed(B_Q) + signed(C_Q) + signed (D_Q);
    when "01" =>
      Y_I <= signed(A_Q) + signed(B_I) - signed(C_Q) - signed (D_I);
      Y_Q <= - signed(A_I) + signed(B_Q) + signed(C_I) - signed (D_Q);
    when "10" =>
      Y_I <= signed(A_I) - signed(B_I) + signed(C_I) - signed (D_I);
      Y_Q <= signed(A_Q) - signed(B_Q) + signed(C_Q) - signed (D_Q);
    when "11" =>
      Y_I <= signed(A_Q) - signed(B_I) - signed(C_Q) + signed (D_I);
      Y_Q <= - signed(A_I) - signed(B_Q) + signed(C_I) + signed (D_Q);
    when others =>
      Y_I <= (others => 'X');
      Y_Q <= (others => 'X');
  end case;
end process;

TWO: TWIDDLE port map (TF, W_I, W_Q);

CMO: CMULT port map (Y_I, Y_Q, W_I, W_Q, S2OUT_I, S2OUT_Q);

end;

```

## 5.7 stage3.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity STAGE3 is
  port (
    RESET      : in  std_logic;
    CLK        : in  std_logic;
    S3HEAD     : in  std_logic;                -- <1,1,u>
    S3IN_I     : in  std_logic_vector(13 downto 0); -- <14,6,t>
    S3IN_Q     : in  std_logic_vector(13 downto 0); -- <14,6,t>
    S3OUTHEAD  : out std_logic;                -- <1,1,u>
    S3OUT_I    : out std_logic_vector(13 downto 0); -- <14,6,t>
    S3OUT_Q    : out std_logic_vector(13 downto 0); -- <14,6,t>
  );
end;

architecture RTL of STAGE3 is

  signal HEAD : std_logic_vector(4 downto 0); -- 5 FFs for Head Signal Delay
  signal COUNT : std_logic_vector(5 downto 0); -- count 0 to 63 cycles
  signal PHASE : std_logic_vector(1 downto 0); -- PHASE 0 to 3
  signal S1, S2, S3 : std_logic;

  signal REGIN_I : std_logic_vector (13 downto 0); -- <14,6,t>
  signal REGIN_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  type shiftreg7 is array (0 to 6) of std_logic_vector (13 downto 0); -- <14,6,t>
  signal REG_I : shiftreg7;
  signal REG_Q : shiftreg7;
  signal A_I, A_Q : std_logic_vector (13 downto 0); -- <14,6,t>
  signal B_I, B_Q : std_logic_vector (13 downto 0); -- <14,6,t>

```

```

signal C_I, C_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal D_I, D_Q : std_logic_vector (13 downto 0); -- <14,6,t>
signal Y_I, Y_Q : std_logic_vector (13 downto 0); -- <14,6,t> butterfly output

begin

-- OUTHEAD GENERATION
process ( CLK, RESET ) begin
    if (RESET = '1') then
        HEAD(0) <= '0';
        HEAD(1) <= '0';
        HEAD(2) <= '0';
        HEAD(3) <= '0';
        HEAD(4) <= '0';
    elsif ( CLK'event and CLK = '1' ) then
        HEAD(0) <= S3HEAD;
        HEAD(1) <= HEAD(0);
        HEAD(2) <= HEAD(1);
        HEAD(3) <= HEAD(2);
        HEAD(4) <= HEAD(3);
    end if;
end process;
S3OUTHEAD <= HEAD(4);

-- 64 CYCLE COUNTER
process ( CLK, RESET ) begin
    if (RESET = '1') then
        COUNT <= "000000";
    elsif ( CLK'event and CLK = '1' ) then
        if (S3HEAD = '1') then
            COUNT <= "000000";
        else
            COUNT <= unsigned(COUNT) + '1';
        end if;
    end if;
end process;

-- PHASE GENERATOR
PHASE <= COUNT(1 downto 0);

-- SELECT SIGNAL GENERATOR
S1 <= PHASE(0) or PHASE(1);
S2 <= PHASE(1);
S3 <= PHASE(0) and PHASE(1);

-- SHIFT REGISTER
process ( CLK ) begin
    if ( CLK'event and CLK = '1' ) then
        REGIN_I <= S3IN_I;   REGIN_Q <= S3IN_Q;
        REG_I(0) <= REGIN_I;  REG_Q(0) <= REGIN_Q;
        REG_I(1) <= REG_I(0); REG_Q(1) <= REG_Q(0);
        REG_I(2) <= REG_I(1); REG_Q(2) <= REG_Q(1);
        REG_I(3) <= REG_I(2); REG_Q(3) <= REG_Q(2);
        REG_I(4) <= REG_I(3); REG_Q(4) <= REG_Q(3);
        REG_I(5) <= REG_I(4); REG_Q(5) <= REG_Q(4);
        REG_I(6) <= REG_I(5); REG_Q(6) <= REG_Q(5);
    end if;
end process;

-- A,B,C,D GENERATION
A_I <= REG_I(3);
A_Q <= REG_Q(3);

```

```

    B_I <= REG_I(0) when S1 = '0' else REG_I(4);
    B_Q <= REG_Q(0) when S1 = '0' else REG_Q(4);
    C_I <= REG_I(1) when S2 = '0' else REG_I(5);
    C_Q <= REG_Q(1) when S2 = '0' else REG_Q(5);
    D_I <= REG_I(2) when S3 = '0' else REG_I(6);
    D_Q <= REG_Q(2) when S3 = '0' else REG_Q(6);

-- RADIX-4 BUTTERFLY

process (PHASE, A_I, B_I, C_I, D_I, A_Q, B_Q, C_Q, D_Q) begin
  case PHASE is
    when "00" =>
      Y_I <= signed(A_I) + signed(B_I) + signed(C_I) + signed (D_I);
      Y_Q <= signed(A_Q) + signed(B_Q) + signed(C_Q) + signed (D_Q);
    when "01" =>
      Y_I <= signed(A_Q) + signed(B_I) - signed(C_Q) - signed (D_I);
      Y_Q <= - signed(A_I) + signed(B_Q) + signed(C_I) - signed (D_Q);
    when "10" =>
      Y_I <= signed(A_I) - signed(B_I) + signed(C_I) - signed (D_I);
      Y_Q <= signed(A_Q) - signed(B_Q) + signed(C_Q) - signed (D_Q);
    when "11" =>
      Y_I <= signed(A_Q) - signed(B_I) - signed(C_Q) + signed (D_I);
      Y_Q <= - signed(A_I) - signed(B_Q) + signed(C_I) + signed (D_Q);
    when others =>
      Y_I <= (others => 'X');
      Y_Q <= (others => 'X');
  end case;
end process;
S3OUT_I <= Y_I;
S3OUT_Q <= Y_Q;

end;

```

## 5.8 reorder.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity REORDER is
  port (
    RESET      : in  std_logic;
    CLK        : in  std_logic;
    ROHEAD     : in  std_logic;           -- <1,1,u>
    ROIN_I     : in  std_logic_vector(13 downto 0); -- <14,6,t>
    ROIN_Q     : in  std_logic_vector(13 downto 0); -- <14,6,t>
    ROOUTHEAD  : out std_logic;           -- <1,1,u>
    ROOUT_I    : out std_logic_vector(13 downto 0); -- <14,6,t>
    ROOUT_Q    : out std_logic_vector(13 downto 0); -- <14,6,t>
  );
end;

architecture RTL of REORDER is

  signal COUNT      : std_logic_vector(5 downto 0);
  signal BANK       : std_logic;           -- Input bank select signal
  signal BANKEN     : std_logic;
  type shiftreg64 is array (0 to 63) of std_logic_vector (13 downto 0); -- <14,6,t>
  signal REGO_I, REGO_Q : shiftreg64;
  signal REG1_I, REG1_Q : shiftreg64;
  signal REGIN_I, REGIN_Q :std_logic_vector (13 downto 0); -- <14,6,t>

```

```

begin

-- 64 CYCLE COUNTER
process ( CLK ) begin
  if (RESET = '1') then
    COUNT <="000000";
    BANKEN <= '0';
  elsif ( CLK'event and CLK = '1' ) then
    if (ROHEAD = '1') then
      COUNT <= "000000";
      BANKEN <= '1';
    elsif (COUNT = "111111") then
      BANKEN <= '0';
    else
      COUNT <= unsigned(COUNT) + '1';
    end if;
  end if;
end process;

-- BANK SELECT GENERATION
process ( CLK ) begin
  if (RESET = '1') then
    BANK <= '0';
  elsif ( CLK'event and CLK = '1' ) then
    if (ROHEAD = '1') then
      BANK <= not BANK;
    end if;
  end if;
end process;

-- INPUT REGISTER
process (CLK) begin
  if (CLK'event and CLK = '1' ) then
    REGIN_I <= ROIN_I;
    REGIN_Q <= ROIN_Q;
  end if;
end process;

-- SHIFT REISTER
process (CLK) begin
  if (CLK'event and CLK = '1' ) then
    if (BANKEN = '1')then
      if (BANK = '0') then
        --
        -- BANK 0 SERIAL INPUT
        --
        for I in 0 to 62 loop
          REGO_I(I) <= REGO_I(I+1);
          REGO_Q(I) <= REGO_Q(I+1);
        end loop;
        REGO_I(63) <= REGIN_I;
        REGO_Q(63) <= REGIN_Q;
        --
        -- BANK 1 REORDER OUPUT
        --
        for I in 0 to 3 loop
          REG1_I(I+ 0) <= REG1_I(I+16);
          REG1_I(I+16) <= REG1_I(I+32);
          REG1_I(I+32) <= REG1_I(I+48);
          REG1_I(I+48) <= REG1_I(I+ 4);
          REG1_I(I+ 4) <= REG1_I(I+20);
        end loop;
      end if;
    end if;
  end if;
end process;

```

```

REG1_I(I+20) <= REG1_I(I+36);
REG1_I(I+36) <= REG1_I(I+52);
REG1_I(I+52) <= REG1_I(I+ 8);
REG1_I(I+ 8) <= REG1_I(I+24);
REG1_I(I+24) <= REG1_I(I+40);
REG1_I(I+40) <= REG1_I(I+56);
REG1_I(I+56) <= REG1_I(I+12);
REG1_I(I+12) <= REG1_I(I+28);
REG1_I(I+28) <= REG1_I(I+44);
REG1_I(I+44) <= REG1_I(I+60);
REG1_Q(I+ 0) <= REG1_Q(I+16);
REG1_Q(I+16) <= REG1_Q(I+32);
REG1_Q(I+32) <= REG1_Q(I+48);
REG1_Q(I+48) <= REG1_Q(I+ 4);
REG1_Q(I+ 4) <= REG1_Q(I+20);
REG1_Q(I+20) <= REG1_Q(I+36);
REG1_Q(I+36) <= REG1_Q(I+52);
REG1_Q(I+52) <= REG1_Q(I+ 8);
REG1_Q(I+ 8) <= REG1_Q(I+24);
REG1_Q(I+24) <= REG1_Q(I+40);
REG1_Q(I+40) <= REG1_Q(I+56);
REG1_Q(I+56) <= REG1_Q(I+12);
REG1_Q(I+12) <= REG1_Q(I+28);
REG1_Q(I+28) <= REG1_Q(I+44);
REG1_Q(I+44) <= REG1_Q(I+60);
end loop;
REG1_I(60) <= REG1_I(1);
REG1_I(61) <= REG1_I(2);
REG1_I(62) <= REG1_I(3);
REG1_Q(60) <= REG1_Q(1);
REG1_Q(61) <= REG1_Q(2);
REG1_Q(62) <= REG1_Q(3);
else
--
-- BANK 1 SERIAL INPUT
--
for I in 0 to 62 loop
REG1_I(I) <= REG1_I(I+1);
REG1_Q(I) <= REG1_Q(I+1);
end loop;
REG1_I(63) <= REGIN_I;
REG1_Q(63) <= REGIN_Q;
--
-- BANK 0 REORDER OUPUT
--
for I in 0 to 3 loop
REGO_I(I+ 0) <= REGO_I(I+16);
REGO_I(I+16) <= REGO_I(I+32);
REGO_I(I+32) <= REGO_I(I+48);
REGO_I(I+48) <= REGO_I(I+ 4);
REGO_I(I+ 4) <= REGO_I(I+20);
REGO_I(I+20) <= REGO_I(I+36);
REGO_I(I+36) <= REGO_I(I+52);
REGO_I(I+52) <= REGO_I(I+ 8);
REGO_I(I+ 8) <= REGO_I(I+24);
REGO_I(I+24) <= REGO_I(I+40);
REGO_I(I+40) <= REGO_I(I+56);
REGO_I(I+56) <= REGO_I(I+12);
REGO_I(I+12) <= REGO_I(I+28);
REGO_I(I+28) <= REGO_I(I+44);
REGO_I(I+44) <= REGO_I(I+60);
REGO_Q(I+ 0) <= REGO_Q(I+16);

```

```

        REGO_Q(I+16) <= REGO_Q(I+32);
        REGO_Q(I+32) <= REGO_Q(I+48);
        REGO_Q(I+48) <= REGO_Q(I+ 4);
        REGO_Q(I+ 4) <= REGO_Q(I+20);
        REGO_Q(I+20) <= REGO_Q(I+36);
        REGO_Q(I+36) <= REGO_Q(I+52);
        REGO_Q(I+52) <= REGO_Q(I+ 8);
        REGO_Q(I+ 8) <= REGO_Q(I+24);
        REGO_Q(I+24) <= REGO_Q(I+40);
        REGO_Q(I+40) <= REGO_Q(I+56);
        REGO_Q(I+56) <= REGO_Q(I+12);
        REGO_Q(I+12) <= REGO_Q(I+28);
        REGO_Q(I+28) <= REGO_Q(I+44);
        REGO_Q(I+44) <= REGO_Q(I+60);
    end loop;
        REGO_I(60) <= REGO_I(1);
        REGO_I(61) <= REGO_I(2);
        REGO_I(62) <= REGO_I(3);
        REGO_Q(60) <= REGO_Q(1);
        REGO_Q(61) <= REGO_Q(2);
        REGO_Q(62) <= REGO_Q(3);
    end if;
end if;
end if;
end process;

-- OUTHEAD GENERATOR
OH1: process (CLK) begin
    if (RESET = '1') then
        ROOUTHEAD <= '0';
    elsif (CLK'event and CLK = '1' ) then
        if (ROHEAD = '1') then
            ROOUTHEAD <= '1';
        else
            ROOUTHEAD <= '0';
        end if;
    end if;
end process;

-- OUTPUT SELECTOR
ROOUT_I <= REG1_I(0) when BANK = '0' else
    REGO_I(0);
ROOUT_Q <= REG1_Q(0) when BANK = '0' else
    REGO_Q(0);

end;

```

## 参考文献

- [1] UNIV. OF THE RYUKYUS LSI DESIGN CONTEST 2007  
| <http://www.ie.u-ryukyu.ac.jp/wada/design07/contest2007.html> —