

CAD  
-report7-

055702B

池野谷克俊

2007年1月30日 火曜日

## 1 正常動作波形

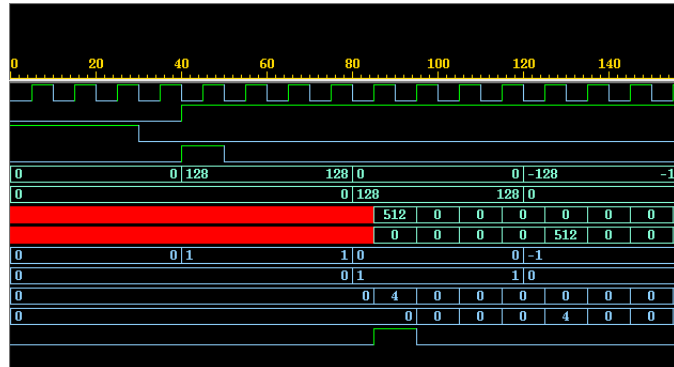


图 1: 正常動作波形

## 2 回路図

 


图 2: 回路図

## 3 Report

```

*****
Report : area
Design : STAGE3
Version: 2003.06
Date   : Thu Jan 25 18:16:00 2007
*****

```

Library(s) Used:

```
class (File: /usr/local/synopsys/U-2003.06-dc/libraries/syn/class.db)
```

```

Number of ports:          61
Number of nets:          1558
Number of cells:         1210
Number of references:    18

Combinational area:      3084.000000
Noncombinational area:  1667.000000
Net Interconnect area:   undefined (Wire load has zero net area)

Total cell area:         4751.000000
Total area:              undefined
1
design_analyzer> report_timing -path full -delay max -max_paths 1 -nworst 1

```

```

*****
Report : timing
        -path full
        -delay max
        -max_paths 1
Design : STAGE3
Version: 2003.06
Date   : Thu Jan 25 18:16:00 2007
*****

```

```

Operating Conditions:
Wire Load Model Mode: top

```

```

Startpoint: COUNT_reg[1]
             (rising edge-triggered flip-flop clocked by CLK)
Endpoint:   COUNT_reg[5]
             (rising edge-triggered flip-flop clocked by CLK)
Path Group: CLK
Path Type:  max

```

Des/Clust/Port	Wire Load Model	Library
STAGE3	20x20	class

Point	Incr	Path
clock CLK (rise edge)	0.00	0.00
clock network delay (ideal)	0.00	0.00
COUNT_reg[1]/CP (FD2)	0.00	0.00 r
COUNT_reg[1]/Q (FD2)	16.29	16.29 r
add_70/plus/A[1] (STAGE3_DW01_inc_6_0)	0.00	16.29 r
add_70/plus/U6/Z (AN3)	1.19	17.48 r
add_70/plus/U9/Z (ND2I)	0.32	17.80 f
add_70/plus/U14/Z (IVI)	0.26	18.06 r
add_70/plus/U15/Z (ND2I)	0.22	18.27 f
add_70/plus/U10/Z (ENI)	0.44	18.72 f
add_70/plus/SUM[5] (STAGE3_DW01_inc_6_0)	0.00	18.72 f
U388/Z (ND2I)	0.27	18.99 r
U207/Z (ND2I)	0.15	19.14 f
COUNT_reg[5]/D (FD2)	0.00	19.14 f
data arrival time		19.14
clock CLK (rise edge)	50.00	50.00
clock network delay (ideal)	0.00	50.00
COUNT_reg[5]/CP (FD2)	0.00	50.00 r
library setup time	-0.85	49.15
data required time		49.15
data required time		49.15
data arrival time		-19.14
slack (MET)		30.01

## 4 テストベンチで計算されている、4FFTの入力値と出力値の関係

入力4点ごとに出力を計算する。ただし、同じ入力値を4回使用して、出力を4つ計算する。計算方法はフェーズごとに若干違う(符号が違う)。正常動作波形での最初の4つ出力値の計算方法を以下に示す。

### 1. フェーズ1

$$S3OUT\_I = 128 + 128 + 128 + 128 = 512$$

$$S3OUT\_Q = 0 + 0 + 0 + 0 = 0$$

### 2. フェーズ2

$$S3OUT\_I = 128 - 128 - 128 + 128 = 0$$

$$S3OUT\_Q = 0 - 0 - 0 + 0 = 0$$

### 3. フェーズ3

$$S3OUT\_I = 128 - 128 + 128 - 128 = 0$$

$$S3OUT\_Q = 0 - 0 + 0 - 0 = 0$$

### 4. フェーズ4

$$S3OUT\_I = 128 + 128 - 128 - 128 = 0$$

$$S3OUT\_Q = 0 + 0 + 0 + 0 = 0$$